



**ESKİŞEHİR TECHNICAL UNIVERSITY**  
**DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING**

**EEM 102 INTRODUCTION TO ELECTRICAL ENGINEERING**

**DC CIRCUIT ANALYSIS**


## DC CIRCUIT ANALYSIS

### OBJECTIVE:

To compare the results of the theoretical and practical analysis of dc circuits.

#### A. Circuit 1:

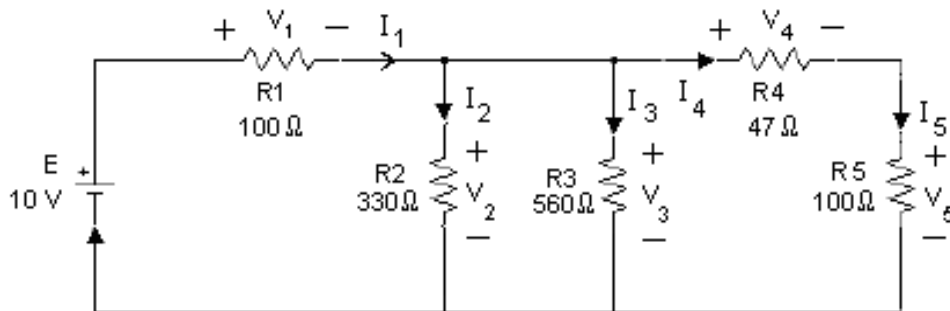
1. Set up the circuit below. Be sure to measure all the resistances and write their values in Table-1 before you insert them into circuit.



2. Measure the voltages  $V_1$ ,  $V_2$ ,  $V_3$ ,  $V_4$ ,  $V_5$  and write them down in Table-1.
3. Measure the currents  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_4$ ,  $I_5$  and write them down in Table-1.
4. Consider the calculated current and voltage values that you found in your preliminary work by using KCL and KVL and write them down in Table-1.

#### B. Circuit 2:

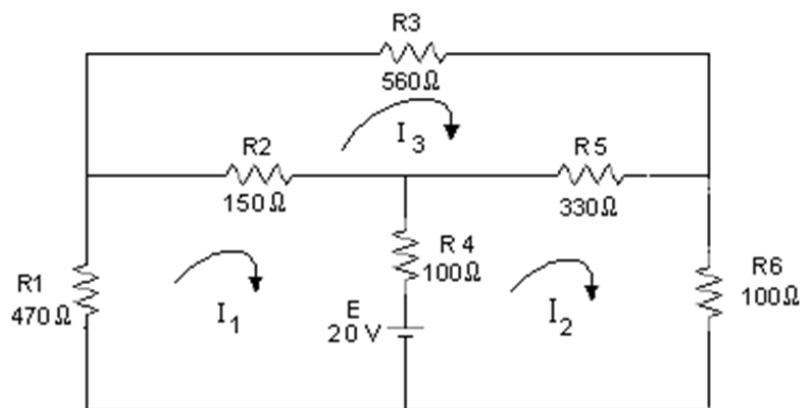1. Set up the circuit below. Be sure to measure all the resistances and write their values in Table-2 before you insert them into circuit.




2. Measure the loop currents  $I_1$ ,  $I_2$ , and  $I_3$  by measuring the currents through  $R_1$ ,  $R_3$  and  $R_6$ . Write them down in Table-3.

3. Consider the measured current values that you found in your preliminary work by using Mesh analysis and write them down in Table-3.

**C. Circuit 3:**

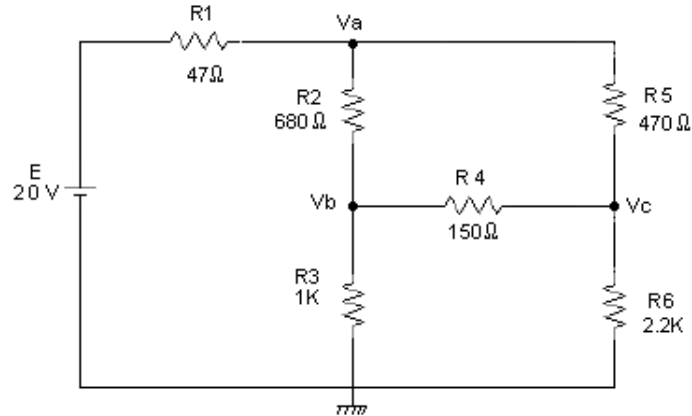1. Set up the circuit below. Be sure to measure all the resistances and write their values in Table-4 before you insert them into circuit.



2. Measure the node voltages  $V_a$ ,  $V_b$ , and  $V_c$  and write them down in Table-5.

3. Consider the node voltage values that you found in your preliminary work by using Nodal analysis and write them down in Table-5.

# EXPERIMENT

## DC CIRCUIT ANALYSIS

Name: .....  
No :.....  
Table No:.....  
Group :.....

# REPORT

TABLE - 1 : Results of Circuit 1

Resistor	Nominal Value	Measured Value	Measured Voltage	Measured Current	Calculated Voltage	Calculated Current
R1						
R2						
R3						
R4						
R5						

1. Explain the differences between the measured and calculated values of currents and voltages.

-----  
-----  
-----  
-----

2. Do the measured values satisfy KCL and KVL? Explain.

-----  
-----  
-----  
-----

TABLE - 2 : Elements of Circuit 2

Resistor	R1	R2	R3	R4	R5	R6
Measured Value						

**TABLE - 3 :** Loop Currents of Circuit 2

<b>Current</b>	<b>Measured Value</b>	<b>Calculated Value</b>
$I_1$		
$I_2$		
$I_3$		

**TABLE - 4:** Elements of Circuit 3

<b>Resistor</b>	<b>R1</b>	<b>R2</b>	<b>R3</b>	<b>R4</b>	<b>R5</b>	<b>R6</b>
Measured Value						

**TABLE - 5 :** Node voltages of Circuit 3

<b>Node Voltage</b>	<b>Measured Value</b>	<b>Calculated Value</b>
$V_a$		
$V_b$		
$V_c$		

Date:				
Table No:	Grades			
Name:	Pre-Lab	Report	Performance	Total
No:				