

ESKISEHIR TECHNICAL UNIVERSITY  
DEPARTMENT OF ELECTRICAL AND ELECTRONICS  
ENGINEERING

**LAB-3**  
**SEQUENTIAL MULTIPLIER**

### 1 Introduction

In this third lab, you will implement an 8-bit sequential multiplier. You have to use the shift and add algorithm whose details will be described in next chapters.

### 2 Binary multiplication

Binary multiplication is similar to decimal multiplication but there is only 1's and 0's.

$$\begin{array}{r}
 230 \leftarrow \text{multiplicand} \rightarrow 0101 \\
 \times 42 \leftarrow \text{multiplier} \rightarrow \times 0111 \\
 \hline
 460 \quad \leftarrow \text{partial products} \rightarrow 0101 \\
 + 920 \quad \leftarrow \text{partial products} \rightarrow 0101 \\
 \hline
 9660 \quad \leftarrow \text{result} \rightarrow + 0000 \\
 \hline
 9660 \quad \leftarrow \text{result} \rightarrow 0100011
 \end{array}$$

$230 \times 42 = 9660$ 
 $5 \times 7 = 35$

While the multiplication is doing, partial products are produced by multiplying a single digit of the multiplier with the entire multiplicand. The shifted partial products are added to get the result. In general, a  $N \times N$  multiplier multiplies two  $N$ -bit numbers and gives a  $2N$ -bit result. The partial products in binary multiplication are either the multiplicand or all 0's since there is only 1's and 0's.

 


Figure 1: Multiplier block diagram

### 3 Sequential Multiplier

A sequential multiplier needs some extra signals for synchronization purpose. You should define these signals in entity section of your design.

**Input clk:** clock signal to synchronize the system.

**Input reset:** asynchronous reset signal to initialize the system.

**Input start:** synchronous signal that must be high to start a new operation.

**Output ready:** synchronous signal that is set during 1 cycle by the multiplier when the result of the operation is available.



Figure 2: Multiplier port declaration.

Shift and add algorithm is as follows; you sequentially multiply the multiplicand (**B**) by each digit of the multiplier (**A**) and then summing up the partial products which are properly shifted to get the final result.

There is an architecture view of the multiplier that you will design.

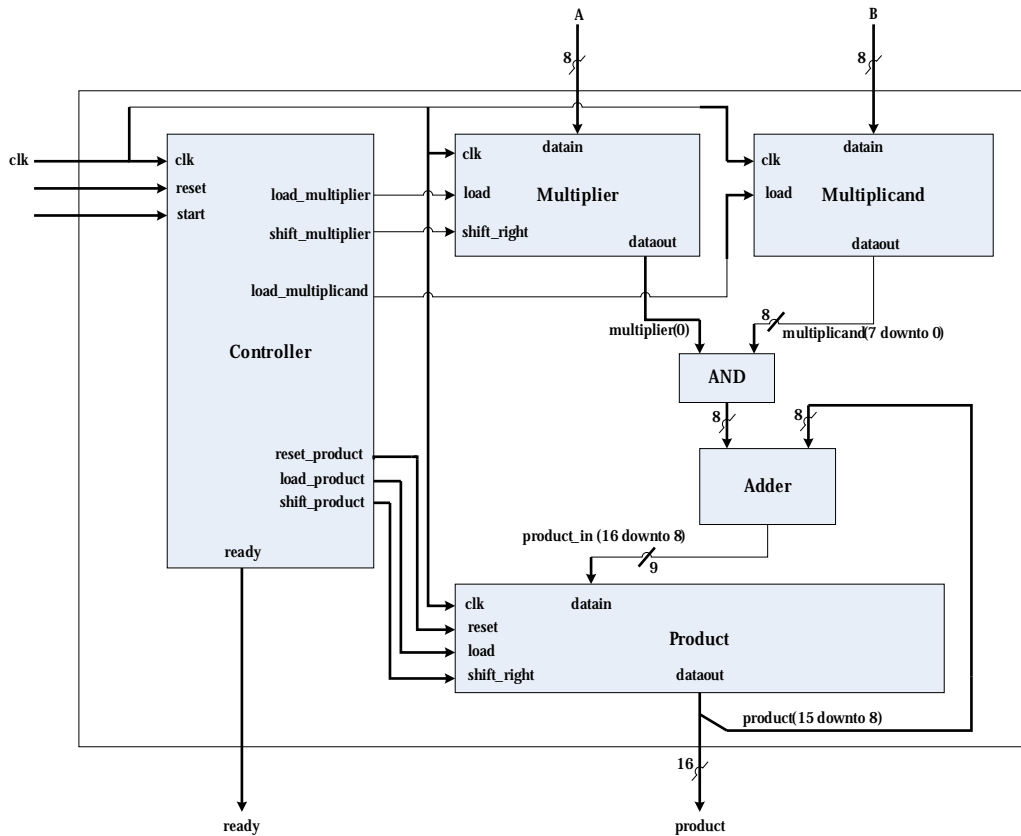


Figure 3: 8-bit Sequential multiplier components

The expressions of the components that you have to implement are listed below.

**8-bit register Multiplicand:**

- Operand B is loaded into internal register inside the multiplicand component when load signal is high.

**8-bit shift register Multiplier:**

- Operand A is loaded into internal register inside the multiplier component when load signal is high.
- Register which keeps the value of A is shifted to the right when shift\_right signal is high.
- The dataout output signal of this component is 1-bit signal. It is the least significant bit of the register.

**17-bit shift register Product:**

- Register is initialized to 0 when reset signal is high.
- Register loads the addition result from adder in its most significant bits when load signal is high.
- Register is shifted to the right when shift input is high.
- The dataout output signal bits are its 16 least significant bits.

**AND component:**

- The block diagram consists of 8 AND gates logically.
- It performs the AND logical operation on each multiplicand bits with the least significant bit of the multiplier.

**8-bit Adder:**


- The component sums the result of the AND gates with the 8 most significant bits of the Product output.

**The system Controller:**

- It includes a state machine and it produces control signals of all other components at right time.
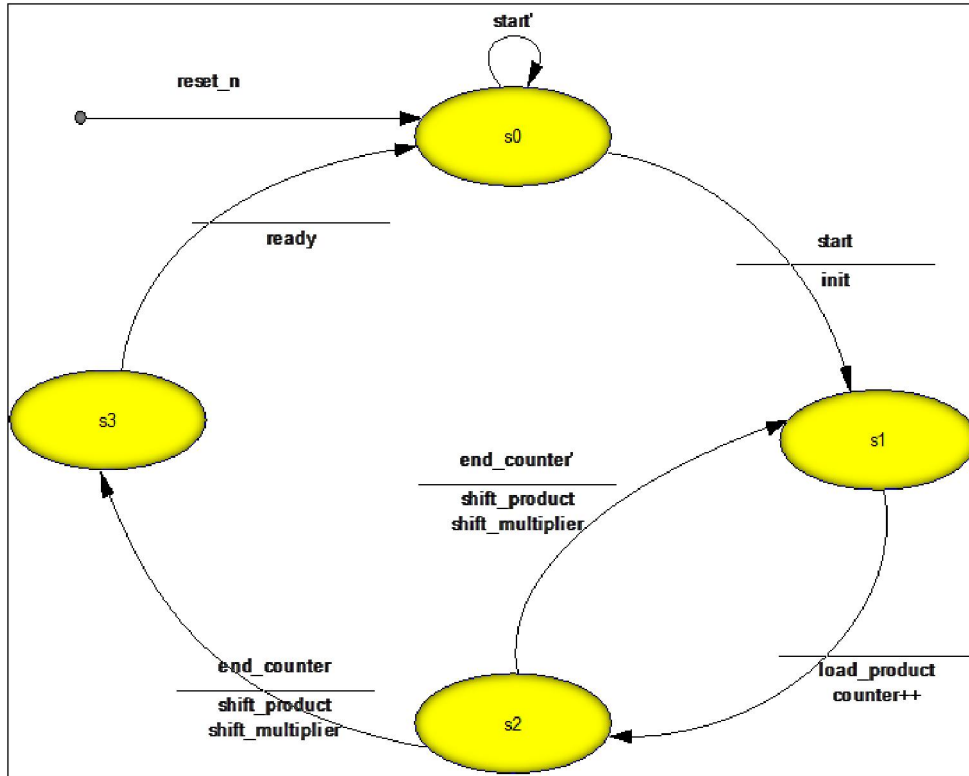
## 4 State Machine

The controller contains the state machine which is given below.



The asynchronous reset signal is initialized to state machine to s0.

**State s0:** Waits in this state till start signal is high before going into state s1 and initializing the register in which:

- The multiplicand and multiplier registers load the input values.
- The product register and the loop counter are initialized to 0.

**State s1:** The next state is always s2.

- In this state, Adder result is loaded into the product register.
- The loop counter is always incremented by 1.

**State s2:** If the loop counter reaches the end value, continue with state s3, otherwise return to the state s1.

- In both cases, the multiplier and product registers are shifted. Therefore, necessary control signals must be produced in this state.

**State s3:** The next state is always s0.

- In this state, multiplication operation is complete. ready output signal must be set active to indicate operation is done.

## **5 Procedure**

In this third lab, you will design a sequential system to perform multiplication operation on two 8-bit operands.

- Write the VHDL description of the multiplication unit whose details are given above.
- You should simulate your design using ISE or another VHDL simulator to prove the correctness of your design.
- There is no hardware implementation for this lab, therefore only your simulation results are graded.