

## Linearity and the Superposition Theorem

We have already talked about linear elements and linear circuits.

Any element with a linear current-voltage (i-v) relationship is linear, including dependent sources.


An important result of linearity is superposition.

Superposition theorem: In any linear circuit containing several independent sources, the voltage or current in any element can be found by adding algebraically the currents or voltages caused by each independent source acting alone while all the other independent sources are killed.

Note: Killing a voltage source means short-circuiting it, killing a current source means open-circuiting it.

Note: Only the independent sources are considered and killed, dependent sources are kept as they are.

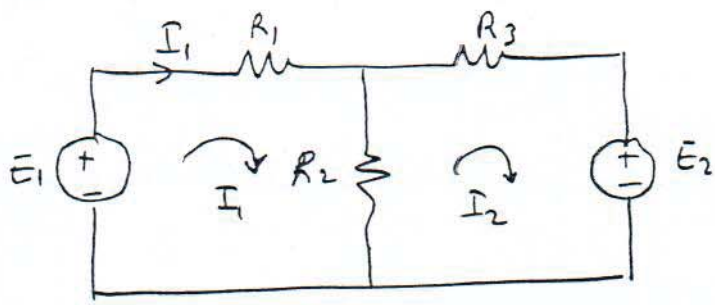Let's look at the circuit below, and obtain the solution for, let's say,  $I_1$ , the current through the resistor  $R_1$ .



$$\begin{aligned} (R_1 + R_2)I_1 - R_2I_2 &= E_1 \\ -R_2I_1 + (R_2 + R_3)I_2 &= -E_2 \end{aligned}$$


$$I_2 = \frac{(R_1 + R_2)I_1 - E_1}{R_2}$$

$$-R_2I_1 + (R_2 + R_3) \frac{(R_1 + R_2)I_1 - E_1}{R_2} = -E_2$$

$$(-R_2^2 + R_1R_2 + R_2^2 + R_1R_3 + R_2R_3)I_1 - (R_2 + R_3)E_1 = -R_2E_2$$


$$I_1 = \underbrace{\frac{R_2 + R_3}{R_1R_2 + R_1R_3 + R_2R_3} E_1}_{\text{Contribution of } E_1} - \underbrace{\frac{R_2}{R_1R_2 + R_1R_3 + R_2R_3} E_2}_{\text{Contribution of } E_2}$$

In fact, with  $E_2 = 0$ :

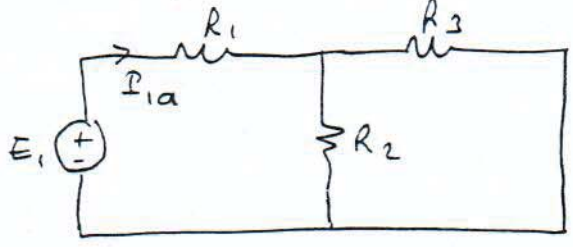

$$I_{1a} = \frac{E_1}{R_1 + \frac{R_2R_3}{R_2 + R_3}} = \frac{R_2 + R_3}{R_1R_2 + R_1R_3 + R_2R_3} E_1$$

with  $E_1 = 0$ :

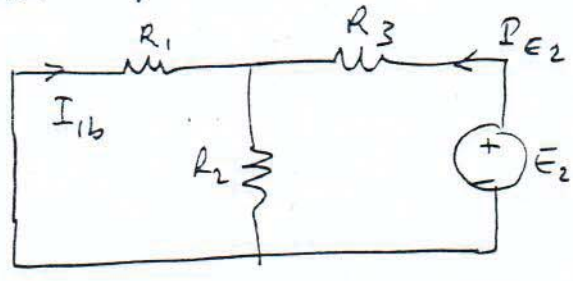


$$I_{E2} = \frac{E_2}{R_3 + \frac{R_1R_2}{R_1 + R_2}} = \frac{R_1 + R_2}{R_1R_2 + R_1R_3 + R_2R_3} E_2$$

$$I_{1b} = -\frac{R_2}{R_1 + R_2} I_{E2} = -\frac{R_2}{R_1R_2 + R_1R_3 + R_2R_3} E_2$$


Note: We do not have to analyze the circuits for each source separately. Sources may be grouped in any convenient way if desired. As long as all the sources are included in the analysis only once, correct solution will be obtained.

Ex

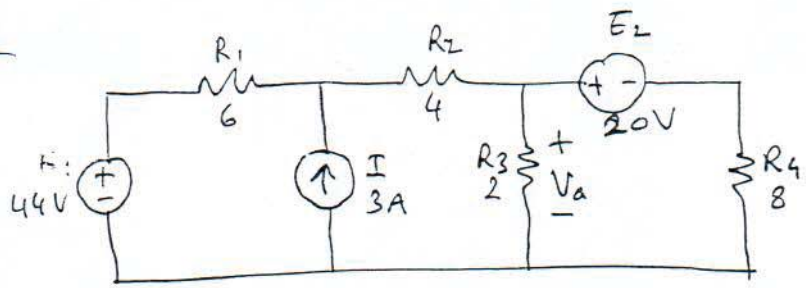

$V_a = ?$

i) With  $E_1$  and  $I$  present:

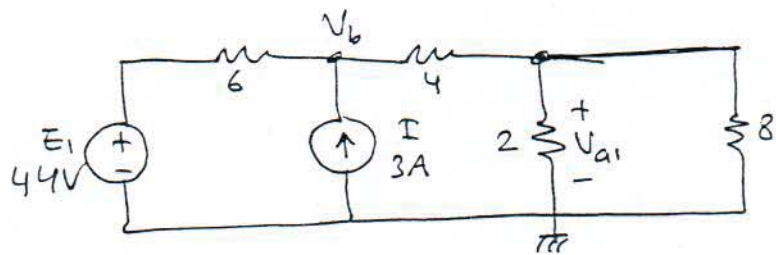

$$\frac{V_b - 44}{6} - 3 + \frac{V_b - V_{a1}}{4} = 0$$

$$\frac{V_{a1} - V_b}{4} + \frac{V_{a1}}{2} + \frac{V_{a1}}{8} = 0$$

$$2V_b - 88 - 36 + 3V_b - 3V_{a1} = 0$$

$$2V_{a1} - 2V_b + 4V_{a1} + V_{a1} = 0$$


$$5V_b - 3V_{a1} = 124$$

$$-2V_b + 7V_{a1} = 0 \rightarrow V_b = 3.5V_{a1}$$

$$17.5V_{a1} - 3V_{a1} = 124$$

$$V_{a1} = \frac{124}{14.5} = \frac{248}{29} \text{ V}$$

ii) With  $E_2$  present:

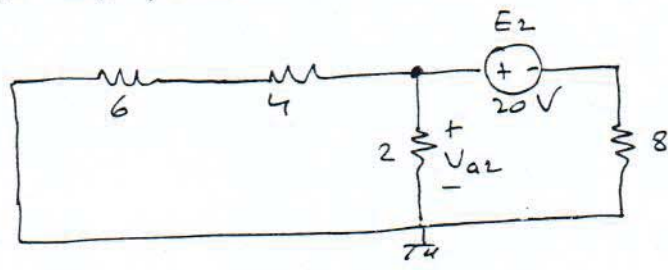

$$\frac{V_{a2}}{6+4} + \frac{V_{a2}}{2} + \frac{V_{a2} - 20}{8} = 0$$


$$4V_{a2} + 20V_{a2} + 5V_{a2} - 100 = 0$$

$$V_{a2} = \frac{100}{29} \text{ V}$$

Hence

$$V_a = V_{a1} + V_{a2} = \frac{248}{29} + \frac{100}{29} = \frac{348}{29} = 12 \text{ V}$$


Ex

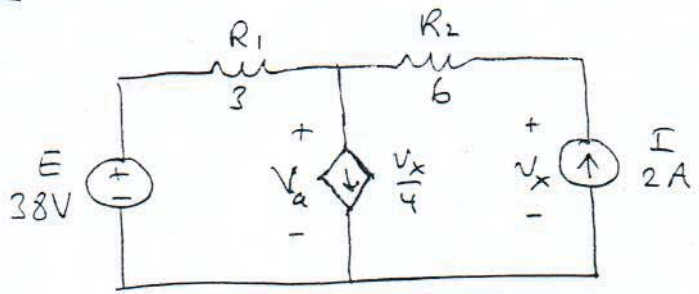

Find  $V_a$  using superposition



With E only (I = 0):

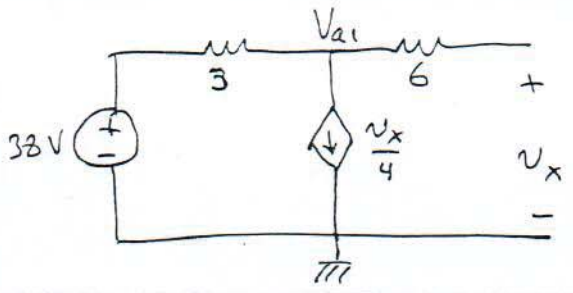


$$v_x = V_{a1}$$

$$\frac{V_{a1} - 38}{3} + \frac{v_x}{4} = 0$$

$$4V_{a1} - 152 + 3V_{a1} = 0$$

$$V_{a1} = \frac{152}{7} \text{ V}$$

With I only (E = 0):

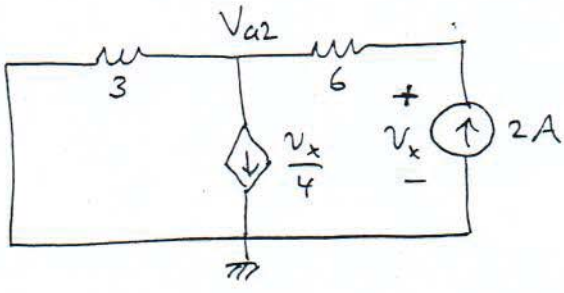

$$\frac{V_{a2}}{3} + \frac{v_x}{4} - 2 = 0$$


$$v_x = V_{a2} + 6 \times 2$$

$$4V_{a2} + 3(V_{a2} + 12) - 24 = 0$$

$$V_{a2} = -\frac{12}{7} \text{ V}$$


Hence  $V_a = V_{a1} + V_{a2} = \frac{152}{7} + \left(-\frac{12}{7}\right) = \frac{140}{7} = 20 \text{ V}$

Ex

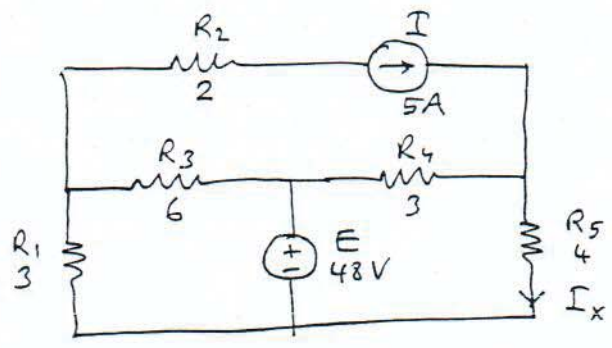


Find  $I_x$  using superposition.

With E only:

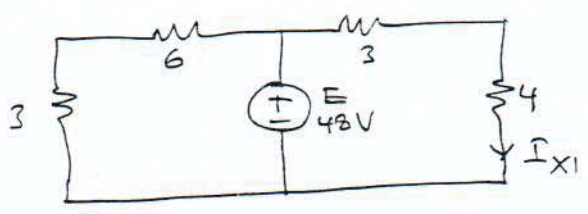

$$I_{x1} = \frac{48}{3+4} = \frac{48}{7} \text{ A}$$

With I only:

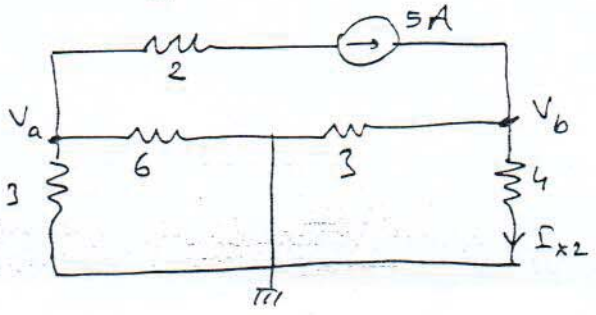

$$\frac{V_b}{3} + \frac{V_b}{4} - 5 = 0$$

$$4V_b + 3V_b = 60 \rightarrow V_b = \frac{60}{7}$$

$$I_{x2} = \frac{15}{7} \text{ A}$$

$$I_x = \frac{48}{7} + \frac{15}{7} = \frac{63}{7} = 9 \text{ A}$$