

## ANALOGIES: CHAPTER 4

- Equations of motion and the behavior of systems involving various physical media are analogous.

- Electrical analogy for thermal, fluid, and mechanical systems are developed.

- Network diagrams are used conveniently employing techniques already available from electrical-network theory

### Analogies between physical media

\* Strong analogies between the equations of motion for lumped physical models of systems in the different physical media.

### Electrical Analog of Heat Conduction

Thermal capacitance  $\approx$  Electrical capacitance:  $C$

Thermal resistance  $\approx$  Electrical resistance:  $R$

### Variables

Through variables: Heat flow  $q \approx$  Electrical current:  $i$

Across variables: Temperature  $T \approx$  Voltage:  $v$ .

Constraints: Prescribed  $T$  (at a boundary)  $\approx$  Prescribed voltage  $v$  (at a node)

Environment  $\equiv$  Temperature source.

Prescribed heat flow  $q$  (through a layer)

$\approx$  prescribed  $i$  (through a branch)

Equilibrium First law of thermodynamics without work

$$\frac{dT}{dt} = \frac{1}{C} q_{net}$$

(applied at a junction without heat storage)  $\approx$  KCL


Temperature compatibility around a path  $\approx$  KVL

Physical relations


Resistance :  $q = \frac{1}{R} (T_a - T_b)$  ;  $i = \frac{1}{R} (V_b - V_a)$

Capacitance:  $q = C \dot{T}$  ;  $i = C \dot{v}$

\* No thermal analog for inductance !

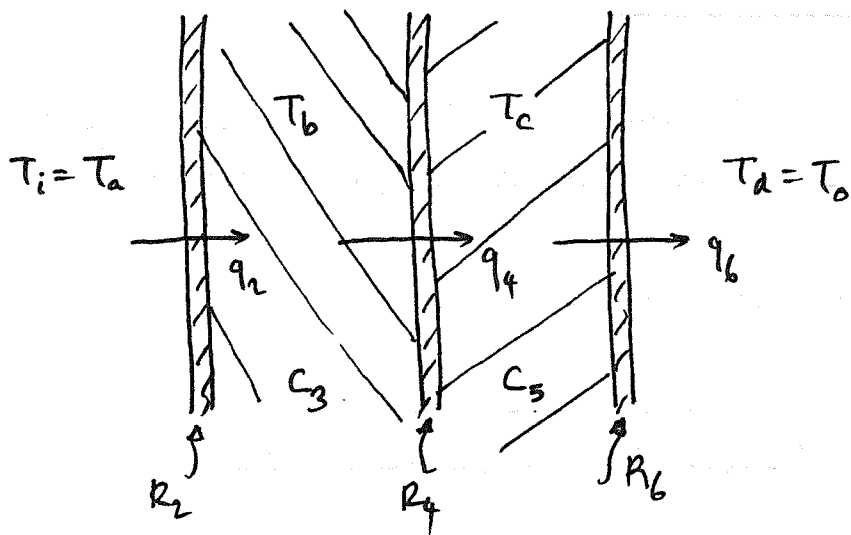

(a) Heat-conduction model

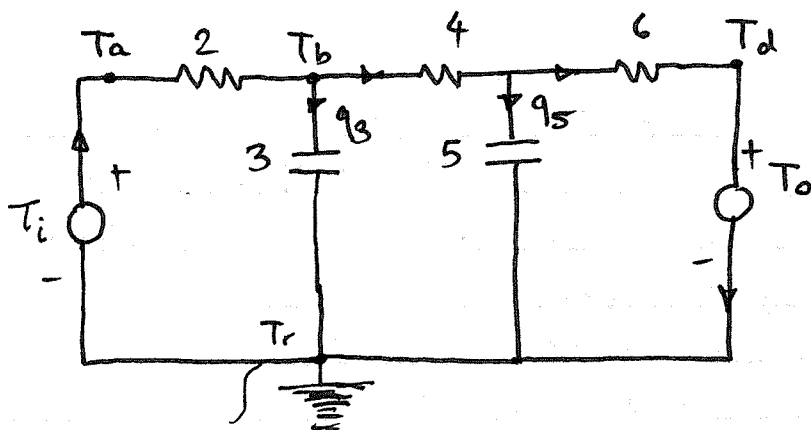

(b) Electrical analog

reference temperature (absolute zero).

Figure. Electrical analog of a heat-conduction system.

- \* Expert in one field can learn the other more easily
- \* It is possible to construct a real electric circuit

whose dynamic behavior will be the same as that of a given heat-flow model.

## Electrical Analogs of Fluid Systems

- Lumped fluid systems only can be represented analogously by electrical networks.

- Body inertia forces are neglected.

### Equations of motion:

Variables and geometry:

Through variables: fluid flow rate  $w \Rightarrow$  current  $i$

Across variables: pressure  $p$  (or reservoir height  $h$ )  $\Rightarrow$  voltage  $v$

Equilibrium: Continuity of flow  $\Rightarrow$  KCL

### Physical relations:

Resistance:

$$w = c_{\alpha} (p_1 - p_2)^{1/\alpha} \quad \& \quad w = c'_{\alpha} (h_1 - h_2)^{1/\alpha}$$

$$\Rightarrow i = \frac{1}{R} v \quad \text{"Ohm's law"} \quad (\alpha=1)$$

$$\alpha \neq 1 \text{ suggests } i = c v^{1/\alpha}$$

Capacitance:

$$\dot{p} = \frac{1}{c} w_{\text{net}} \quad \& \quad \dot{h} = \frac{1}{c} w_{\text{net}}$$

$$\Rightarrow \dot{v} = \frac{1}{C} i$$

# Electrical Analog of Mechanical Systems

Two analogies are possible

$u$  (velocity)  $\rightarrow v$  (voltage)  
 $f$  (force)  $\rightarrow i$  (current)

$\left. \begin{array}{l} \\ \end{array} \right\}$  Consistent with the previous developments since through and across variables are mapped to the through and across variables!

or

$f \rightarrow v$  and  $u \rightarrow i$

## Variables





Through variables:  $f \rightarrow i$   
 Across variables:  $u \rightarrow v$

## Equilibrium

$$\begin{aligned} \sum f^* &= 0 & \approx & \sum i = 0 \text{ (for a node)} \\ \sum M^* &= 0 & \approx & \end{aligned}$$

Geometric compatibility  $\approx$  KVL.

## Physical relations

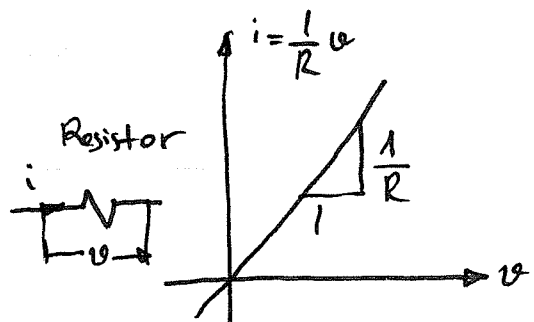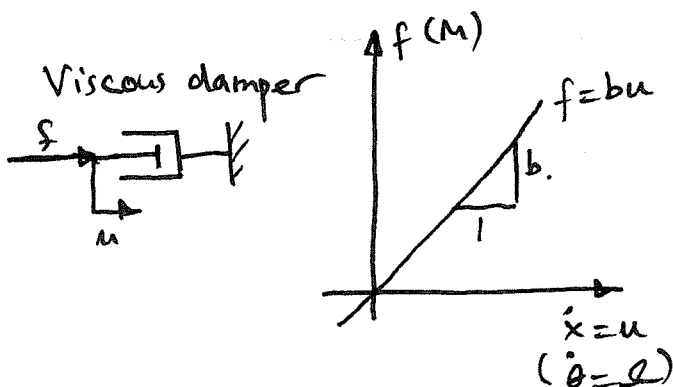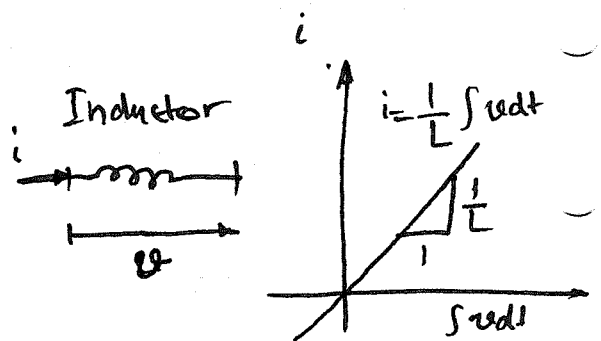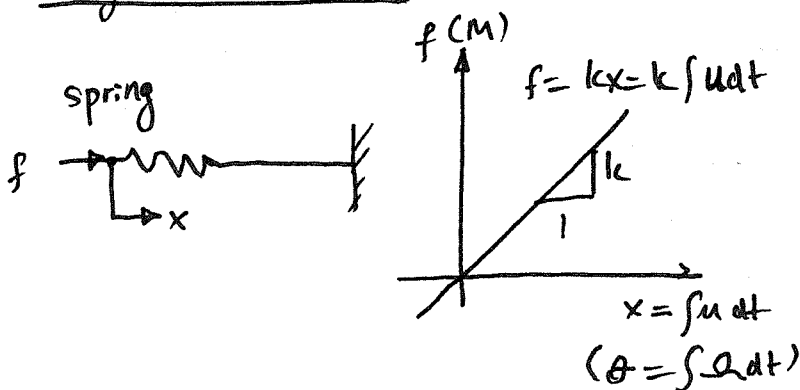


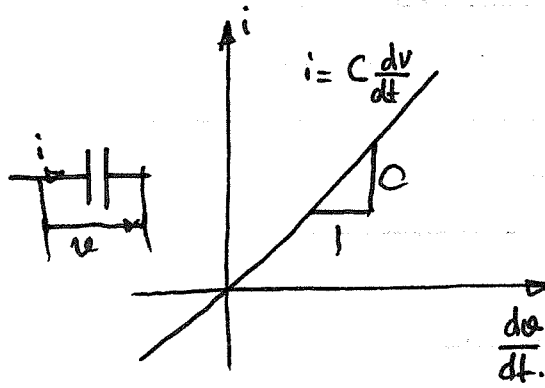
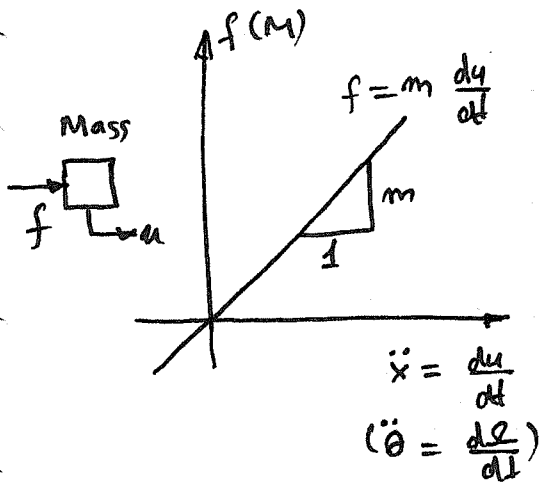


Figure. The physical basis for mechanical-electrical analogy

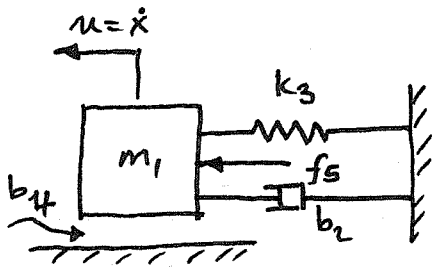
Example: Electrical analog for a simple mechanical system



One degree-of-freedom

$$u_1 = u_2 = u_3 = u_4 = u$$

$f_s$  specified


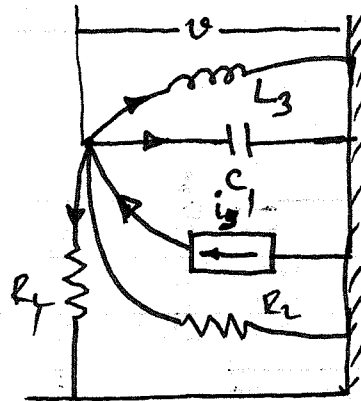


One node; one independent voltage

$$v_1 = v_2 = v_3 = v_4 = 0$$

$i_5$  specified

Equilibrium

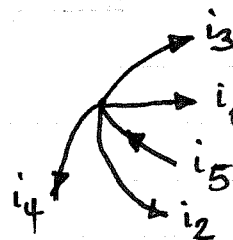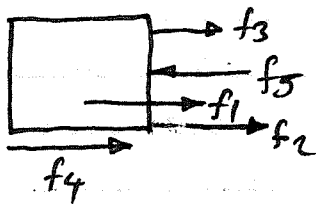

$$\sum f^* = 0: -f_5 + f_1 + f_2 + f_3 + f_4 = 0$$

$$\text{KCL: } -i_5 + i_1 + i_2 + i_3 + i_4 = 0$$

Physical relations:

$$f_1 = m_1 \dot{u}_1$$

$$f_2 = b_2 u_2$$

$$f_3 = k_3 \int u_3 dt$$

$$f_4 = b_4 u_4$$

$$i_1 = C_1 \dot{v}_1$$

$$i_2 = \frac{1}{R_2} v_2$$



$$i_3 = \frac{1}{L_3} \int v_3 dt$$

$$i_4 = \frac{1}{R_4} v_4$$

$$f_5 = m_1 \dot{u} + b_2 u + k_3 \int u dt + b_4 u$$

$$i_5 = C_1 \dot{v} + \frac{1}{R_2} v + \frac{1}{L_3} \int v dt + \frac{1}{R_4} v$$

Example. A more complex system

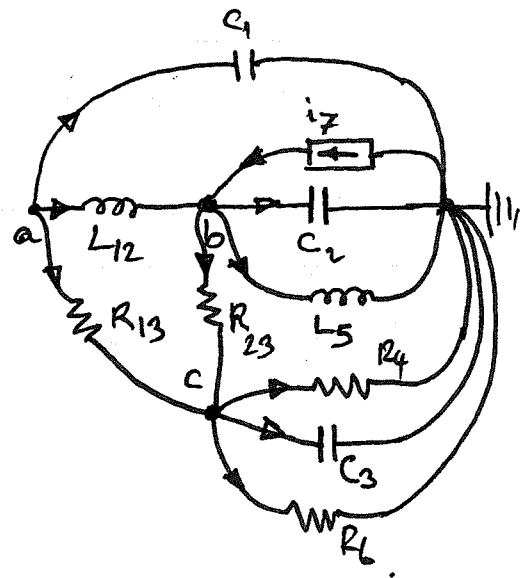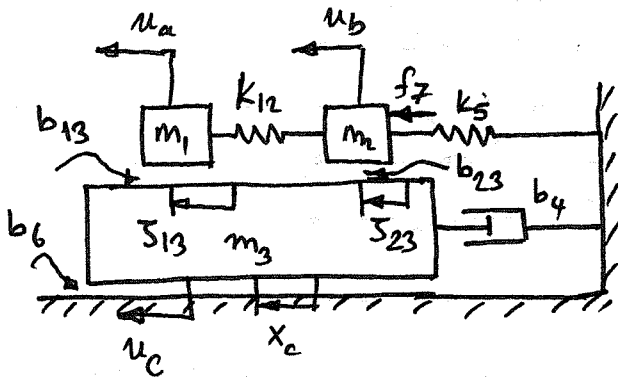

Three degree-of-freedom

$$\dot{s}_{12} = u_a - u_b$$

$$\dot{s}_{13} = u_a - u_c$$

$$\dot{s}_{23} = u_b - u_c$$

$$u_1 = u_a$$

$$u_2 = u_5 = u_b$$

$$u_3 = u_4 = u_6 = u_c$$

Three independent node voltages


$$v_{12} = u_a - u_b \quad v_1 = u_a$$

$$v_{13} = u_a - u_c \quad v_2 = u_5 = u_b$$


$$v_{23} = u_b - u_c, \quad v_3 = u_4 = u_6 = u_c$$

# Equilibrium

(i) Free-body diagrams

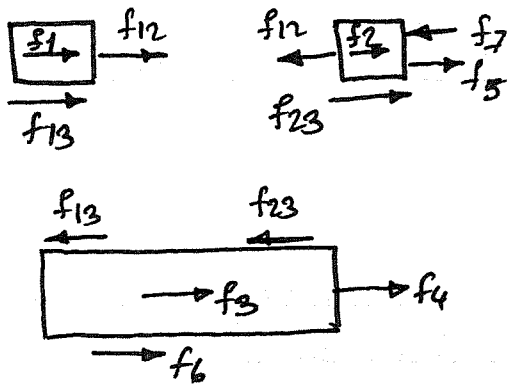

(i) Isolate nodes

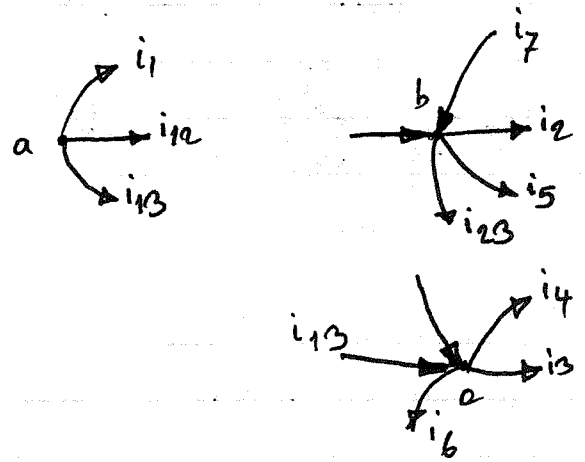

(ii) Force balance ( $\sum f^* = 0$ )

mass  $m_1$  :  $f_1 + f_{12} + f_{13} = 0$

mass  $m_2$  :  $-f_2 - f_{12} + f_5 + f_{23} = 0$

mass  $m_3$  :  $-f_{13} - f_{23} + f_3 + f_4 + f_6 = 0$

(ii) KCL ( $\sum i_{out} = 0$ )

Node a :  $i_1 + i_{12} + i_{13} = 0$

Node b :  $-i_7 - i_2 + i_5 + i_{23} = 0$

Node c :  $-i_{13} - i_{23} + i_3 + i_4 + i_6 = 0$

Physical relations :

$f_2 = m_2 \dot{u}_2$

$f_{23} = b_{23} \dot{s}_{23}$

⋮


$i_2 = C_2 \dot{v}_2$

$i_{23} = \frac{1}{R_{23}} v_{23}$

⋮

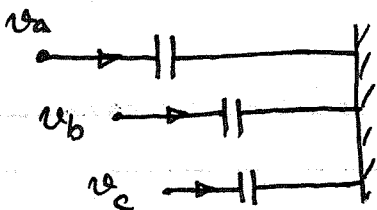
## Construction Procedure

Place first node voltages representing independent velocities and between node voltages and the ground voltages place capacitances representing inertias. Then, distribute other elements between.



"Capacitans, representing masses must always be connected to ground"
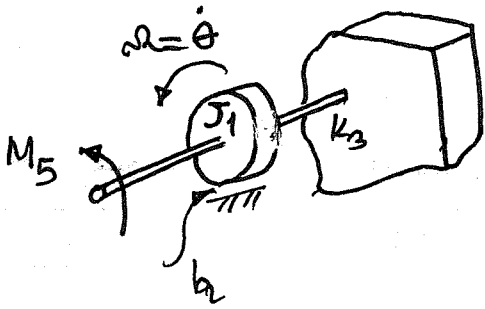
## Electrical analogy for rotary mechanical systems




$$M_5 = J_1 \dot{\omega} + b_2 \omega + k_3 \int \omega dt$$

"Similar to analogy developed for translational mechanical systems"  
 $F \rightarrow m$ ,  $x \rightarrow \theta$ ,  $u \rightarrow \omega$  (Substitutions)

## Mechanical motions in two or three dimensions:

- Development of electrical analogs more sophisticated!
- Too cumbersome to be useful!
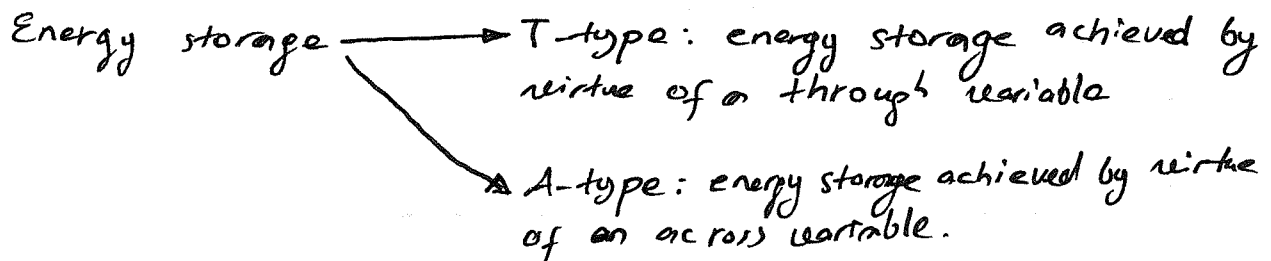
## Classification of Dynamic System Elements



Sources: T or A-types.

Energy-dissipation elements.

## Benefits and Limitations of analysis by analogy

- Additional insight into the behavior of a system might be gained by considering its analog.
- They prevent us from thinking about new physical phenomena or when they cause us to force a system arbitrarily into a mold of analysis which it does not fit.