

AVERAGE POWER AND EFFECTIVE VALUES

Average Power: For a periodic function with period T , the average value is given as

$$P = \frac{1}{T} \int_{t_x}^{t_x+T} p(t) dt$$

or

$$P = \frac{1}{nT} \int_{t_x}^{t_x+nT} p(t) dt = \frac{1}{nT} \int_{-nT/2}^{nT/2} p(t) dt = \lim_{n \rightarrow \infty} \frac{1}{nT} \int_{-nT/2}^{nT/2} p(t) dt$$

Replacing nT by the continuous variable τ

$$P = \lim_{\tau \rightarrow \infty} \frac{1}{\tau} \int_{-\tau/2}^{\tau/2} p(t) dt$$

Now, let's look at general case. We can write

$$v(t) = V_m \cos(\omega t + \alpha)$$

$$i(t) = I_m \cos(\omega t + \beta) = I_m \cos(\omega t + \alpha - \theta)$$

for any element. Note that $\beta = \alpha - \theta \rightarrow \theta = \alpha - \beta$ is the phase angle by which the voltage leads the current.

$$p(t) = v(t) \cdot i(t) = V_m I_m \cos(\omega t + \alpha) \cos(\omega t + \alpha - \theta)$$

Using the identity $\cos a \cdot \cos b = \frac{1}{2} [\cos(a-b) + \cos(a+b)]$

$$p(t) = \frac{1}{2} I_m V_m [\cos \theta + \cos(2\omega t + 2\alpha - \theta)]$$

$$P = \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m [\cos \theta + \cos(2\omega t + 2\alpha - \theta)] dt$$

$$= \frac{V_m I_m}{2} \cdot \frac{1}{T} \cos \theta \int_0^T dt + \frac{V_m I_m}{2T} \int_0^T \cos(2\omega t + 2\alpha - \theta) dt$$

$$P = \frac{1}{2} V_m I_m \cos \theta$$

Case 1: For an ideal resistor, $v = Ri$, and $\theta = 0^\circ$ (I-2)

$$P_R = \frac{1}{2} V_m I_m \cos 0^\circ = \frac{1}{2} V_m I_m = \frac{1}{2} R I_m^2 = \frac{1}{2} \frac{V_m^2}{R}$$


Case 2: For an ideal reactive element $\theta = \mp 90^\circ$,

$$P_x = 0$$

Ex: Let $Z = 5 + j3$ and $\vec{I} = 2 \angle 25^\circ$ A, then

$$P = \frac{1}{2} \cdot 5 \cdot 2^2 = 10 \text{ W}$$

Maximum Power Transfer:

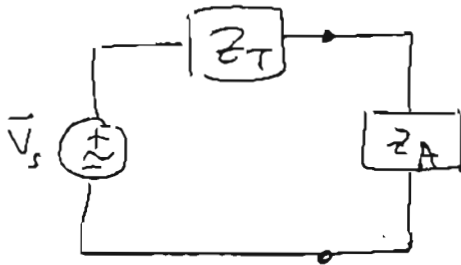

$$Z_T = R_T + jX_T$$

$$Z_A = R_A + jX_A$$

For maximum power transfer,

$$X_A = -X_T \text{ and } R_A = R_T, \text{ or}$$

$$Z_A = Z_T^*$$

Power for cases where $i(t)$ is not periodic:

Let $i(t) = \cos t + \cos \sqrt{2}t$ and $R = 1 \Omega$. Then

$$P = \lim_{T \rightarrow \infty} \frac{1}{2} \int_{-T/2}^{T/2} (\cos^2 t + 2 \cos t \cdot \cos \sqrt{2}t + \cos^2 \sqrt{2}t) dt$$

$$= \lim_{T \rightarrow \infty} \frac{1}{2} \int_{-T/2}^{T/2} \cos^2 t dt + \lim_{T \rightarrow \infty} \frac{1}{2} \int_{-T/2}^{T/2} \cos t \cdot \cos \sqrt{2}t dt$$

$$+ \lim_{T \rightarrow \infty} \frac{1}{2} \int_{-T/2}^{T/2} \cos^2 \sqrt{2}t dt$$

The middle term's integrand can be expressed as

$$\frac{1}{2} [\cos (1+\sqrt{2})t + \cos (1-\sqrt{2})t]$$

and will result in zero when integrated.

$$P = \frac{1}{2} + 0 + \frac{1}{2} = 1 \text{ W}$$

20 "EK"

We can generalize this result.

(I-3)

$i(t) = I_{m1} \cos \omega_1 t + I_{m2} \cos \omega_2 t + \dots + I_{mn} \cos \omega_n t$
will deliver an average power, to a resistor R , of

$$P = \frac{1}{2} (I_{m1}^2 + I_{m2}^2 + \dots + I_{mn}^2) R$$

Note: The sinusoids should be at different frequencies to use the above formula.

Ex: $R = 5 \Omega$, $i(t) = 4 \cos 2t - 6 \cos 4t$

$$P = \frac{1}{2} (4^2 + 6^2) 5 = 130 \text{ W}$$

If $i(t) = 4 \cos 2t - 6 \cos 2t$, then

$$i(t) = -2 \cos 2t$$


$$P = \frac{1}{2} (2^2) 5 = 10 \text{ W}$$

Note: The last function can be expressed in infinitely many different ways. Such as

$$i(t) = 999998 \cos 2t - 1000000 \cos 2t$$


This would not mean, we can obtain a very large power $[P \neq \frac{1}{2} (999998^2 + 1000000^2) R]$.

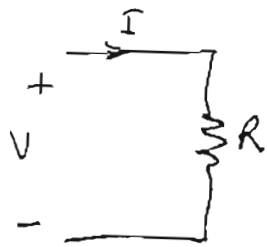Effective values of current and voltage :



DC Case

$$P = RI^2$$

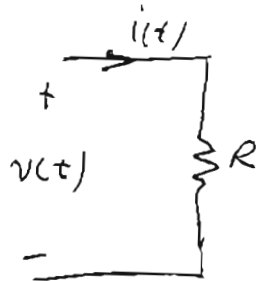

AC case

$$P = \frac{1}{T} \int_0^T Ri^2 dt$$

The question is "Can we express the average power in a similar fashion to DC case?"

$P = \frac{1}{T} \int_0^T Ri^2 dt = RI_e^2$ where I_e is the effective value of the current. Then

$$I_e = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

Similarly

$$V_e = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

* The effective values are also called rms values (root-mean-square).

Ex $i(t) = I_m \cos(\omega t + \beta)$, $\omega = \frac{2\pi}{T}$

$$I_e = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t + \beta) dt} = \sqrt{\frac{I_m^2}{2T} \int_0^T [1 + \cos(2\omega t + 2\beta)] dt}$$

$$= \sqrt{\frac{I_m^2}{2T} \left[t + \frac{\sin(2\omega t + 2\beta)}{2\omega} \right]_0^T} = \sqrt{\frac{I_m^2}{2T} \left[T + \frac{\sin(2\omega T + 2\beta) - \sin 2\beta}{2\omega} \right]}$$

$$= \sqrt{\frac{I_m^2}{2T} \left[T + \frac{\sin 2\beta - \sin 2\beta}{2\omega} \right]} = \frac{I_m}{\sqrt{2}}$$

Then

(I-5)

$$P = \frac{1}{2} R I_m^2 = R I_e^2 = V_e I_e = \frac{V_e^2}{R}$$

The general expression for average power will be

$$P = \frac{1}{2} V_m I_m \cos \theta = V_e I_e \cos \theta$$

Ex: The voltage we use in homes is $220 V_{rms}$ in Turkey. What is its peak value?

$$V_m = \sqrt{2} V_e = \sqrt{2} \cdot 220 = 311 \text{ V}$$

* Phasor currents and voltages can also be expressed with ^{their} effective values.

$$\vec{I} = 34 \angle 20^\circ \text{ A} \rightarrow \vec{I}_e = \frac{34}{\sqrt{2}} \angle 20^\circ \text{ A}_{rms}$$

Note: ~~Effective~~ currents which are the sum of sinusoidal currents with different frequencies will have an effective value of

$$I_e = \sqrt{I_{1e}^2 + I_{2e}^2 + \dots + I_{ne}^2}$$

Apparent Power:

If $v(t) = V_m \cos(\omega t + \alpha)$ and $i(t) = I_m \cos(\omega t + \beta)$ with $\theta = \alpha - \beta$, then we know that

$$P = \frac{1}{2} V_m I_m \cos \theta = V_e I_e \cos \theta$$

The product $V_e I_e$ is called the apparent power, since it is the maximum power that can be obtained from the circuit, $\cos \theta = 1$ is the maximum value of $\cos \theta$.


That is, $V_e I_e$ is the apparent power, because the actual power that will be obtained depends on $\cos \theta$.

Power Factor :

$$P.F. = \frac{\text{average power}}{\text{apparent power}} = \frac{P}{V_e I_e} = \cos \theta$$

θ = power factor angle

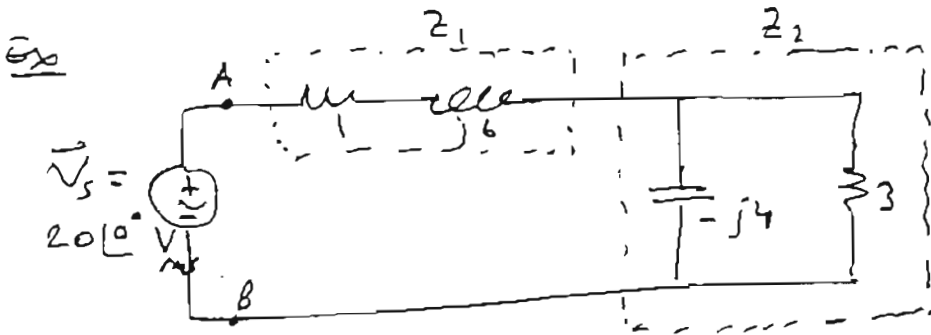Note : For a given PF, we would not be able to tell if θ is positive or negative. Hence load type should also be specified when giving PF. Such as PF = 0.8 inductive



$$Z_1 = 1 + j6$$

$$Z_2 = \frac{3(-j4)}{3 - j4} = \frac{-j12}{3 - j4}$$

$$= \frac{-j12(3 + j4)}{3^2 + 4^2}$$

$$= 1.92 - j1.44$$

$$Z_{AB} = 1 + j6 + 1.92 - j1.44 = 2.92 + j4.56$$

$$\vec{I} = \frac{20 \angle 0^\circ}{2.92 + j4.56} = \frac{20 \angle 0^\circ}{5.41 \angle 57.4^\circ} = 3.70 \angle -57.4^\circ$$

$$P_s = (20)(3.70) \cos [0 - (-57.4^\circ)] = 74 \cos 57.4^\circ = 39.9 \text{ W}$$

$$PF = \cos 57.4^\circ = 0.54 \text{ Inductive}$$

Note : $Z_{AB} = 5.41 \angle 57.4^\circ$, hence $PF = \cos 57.4^\circ = 0.54$

$$\text{since } Z_{AB} = \frac{\vec{V}_s}{\vec{I}} = \left| \frac{\vec{V}_s}{\vec{I}} \right| \angle \theta$$

Complex Power :

$$P = I_e V_e \cos \theta = I_e V_e \cos (\alpha - \beta) = I_e V_e \cdot RE \left[e^{j(\alpha - \beta)} \right]$$

$$= RE \left[I_e V_e e^{j(\alpha - \beta)} \right] = RE \left[I_e e^{-j\beta} \cdot V_e e^{j\alpha} \right]$$

$$= RE \left[\vec{I}_e^* \cdot \vec{V}_e \right]$$

$$S = \text{Complex power} = \vec{V}_e \vec{I}_e^*$$

$$|S| = V_e I_e = \text{apparent power}$$

$$\angle S = \alpha - \beta = \theta = \text{P.F. angle}$$

and written in Cartesian coordinates:

$$S = \vec{V}_e \vec{I}_e^* = V_e I_e e^{j(\alpha - \beta)} = V_e I_e e^{j\theta}$$

$$= V_e I_e \cos \theta + j V_e I_e \sin \theta$$


$$= P + jQ$$

↑ average power ↑ reactive power (VAR)

Note: $\vec{I}_e = I_e \cos \theta + j I_e \sin \theta = \vec{I}_{e1} + \vec{I}_{e2}$ where
 \vec{I}_{e1} is the in phase component with \vec{V}_e and
 \vec{I}_{e2} is the 90° out of phase (perpendicular)
 component of \vec{I}_e . Hence

$$P = |\vec{V}_e \cdot \vec{I}_{e1}| \quad \text{and} \quad Q = |\vec{V}_e \cdot \vec{I}_{e2}|$$

Complex Power in Load Combinations:

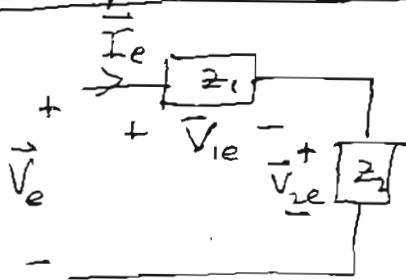


$$\vec{V}_e = \vec{V} + \vec{V}$$

$$S = \vec{V}_e \vec{I}_e^* = (\vec{V}_{1e} + \vec{V}_{2e}) \vec{I}_e^*$$

$$= \vec{V}_{1e} \vec{I}_e^* + \vec{V}_{2e} \vec{I}_e^*$$

$$= S_1 + S_2$$

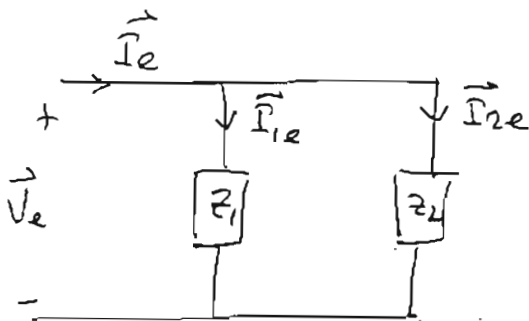


$$\vec{I}_e = \vec{I}_{1e} + \vec{I}_{2e}$$

$$S = \vec{V}_e \vec{I}_e^* = \vec{V}_e (\vec{I}_{1e} + \vec{I}_{2e})^*$$

$$= \vec{V}_e \vec{I}_{1e}^* + \vec{V}_e \vec{I}_{2e}^*$$

$$= S_1 + S_2$$

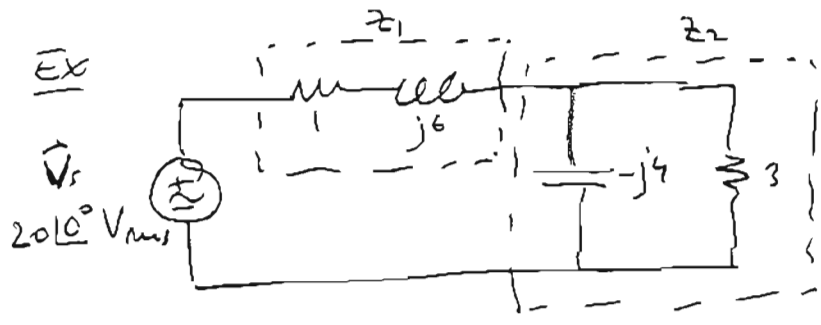

$$Z_1 = 1 + j6$$

$$Z_2 = \frac{3(-j4)}{3 - j4} = \frac{-j12}{3 - j4}$$

$$= \frac{-j12(3 + j4)}{25} = 1.92 - j1.44$$

$$Z_{AB} = 1 + j6 + 1.92 - j1.44 = 2.92 + j4.56 \Omega$$

$$\vec{I}_s = \frac{20 \angle 0^\circ}{2.92 + j4.56} = \frac{20 \angle 0^\circ}{5.41 \angle 57.5^\circ} = 3.69 \angle -57.5^\circ \text{ A}_{rms}$$

$$S_s = 20 \angle 0^\circ \cdot (3.69 \angle 57.5^\circ) = 73.8 \angle 57.5^\circ = 39.8 + j62.2$$

$$P_s = 39.8 \text{ W}, \quad Q_s = 62.2 \text{ VAR}$$

$$S_{Z_1} = \vec{V}_{Z_1} \vec{I}_{Z_1}^* = Z_1 \vec{I}_{Z_1} \vec{I}_{Z_1}^* = Z_1 |\vec{I}_{Z_1}|^2$$

$$= (1 + j6) (3.69)^2 = 13.6 + j81.7$$

$$S_{Z_2} = (1.92 - j1.44) (3.69)^2 = 26.1 - j19.6$$

Hence $P_{Z_1} = 13.6 \text{ W}, P_{Z_2} = 26.1 \text{ W}, P_{Total} = 13.6 + 26.1 = 39.7 \text{ W} = P_s$

$$Q_{Z_1} = 81.7 \text{ VAR}, \quad Q_{Z_2} = -19.6 \text{ VAR}$$

$$Q_{Total} = 81.7 - 19.6 = 62.1 \text{ VAR} = Q_s$$


Ex: A load draws 1 kW under a PF = 0.65 inductive from a source of $\vec{V}_e = 220 \angle 0^\circ \text{ V}_{rms}$, $f = 50 \text{ Hz}$. What should be done to raise the PF to 0.95 inductive?

$$S_1 = 1000 + j \frac{1000}{0.65} \cdot \sin(\cos^{-1} 0.65)$$

$$= 1000 + j1169$$

* To obtain PF = 0.95, we need to have $\theta = \cos^{-1} 0.95 = 18.2^\circ$. There are 2 possible solutions:

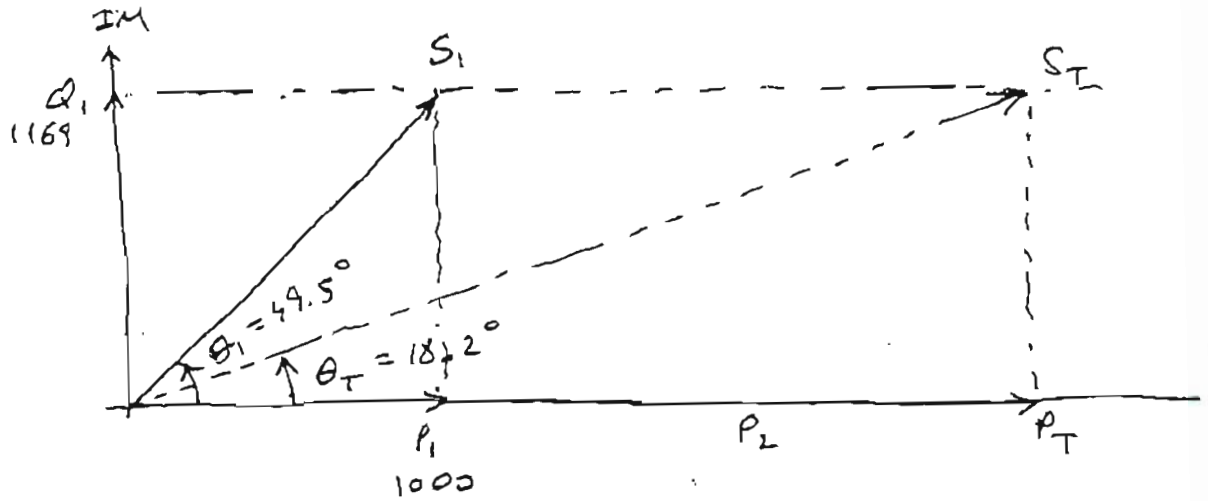1) Increase P_1 while keeping Q_1 constant.




$$|S_T| = \frac{1169}{\sin 18.2^\circ} = 3743$$

$$S_T = 3743 (0.95) + j1169 = 3556 + j1169$$

Then $P_2 = 3556 - 1000 = 2556$ W. A resistive element has to be added to the system to use (waste?) this power. So, this is not a good solution.

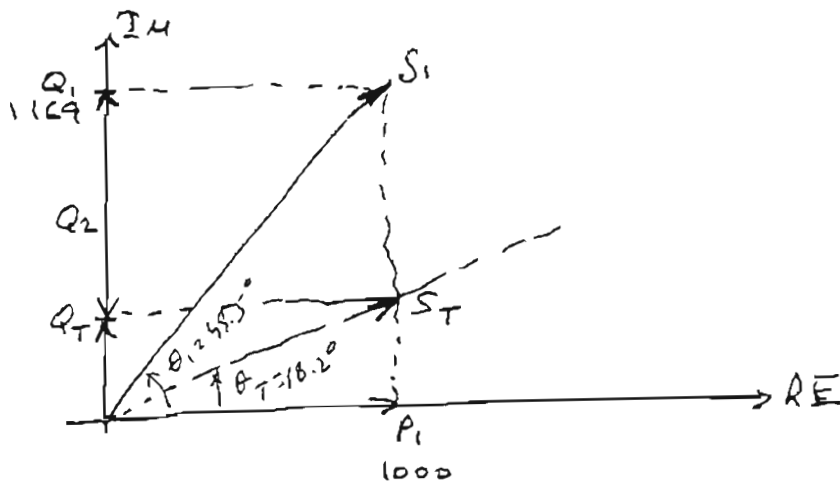2) Decrease Q_1 while keeping P_1 constant.



$$S_T = 1000 + j \frac{1000}{0.95} \sqrt{1 - 0.95^2} = 1000 + j329$$

$$Q_2 = j329 - j1169 = -j840 = \vec{V}_2 \vec{I}_2^*$$

$$\vec{I}_2^* = \frac{-j840}{220 \angle 0^\circ} = -j3.82 \rightarrow \vec{I}_2 = j3.82 \text{ A}_{rms}$$

$$Z_2 = \frac{220 \angle 0^\circ}{j3.82} = -j57.62 \Omega$$

$$C = \frac{1}{2\pi \cdot 50 (57.62)} = 55.3 \times 10^{-6} \text{ F}$$

$C = 55.3 \mu\text{F}$ should be connected in parallel with the load. This operation is called "compensation". If the PF of a load is below 0.8, then this is penalized by charging a higher rate per kWh.

The current drawn from the line in the original case is

$$\vec{I}_1 = \left[\frac{S_1}{\vec{V}_e} \right]^* = \left[\frac{1000 + j1169}{220} \right]^* = 6.99 \angle -49.5^\circ \text{ A}_{\text{rms}}$$

The current after compensation is

$$\vec{I}_T = \left[\frac{S_T}{\vec{V}_e} \right]^* = \left[\frac{1000 + j329}{220} \right]^* = 4.76 \angle -18.2^\circ \text{ A}_{\text{rms}}$$

Let's assume a value for the resistance of the line the power is carried over, say 10Ω . Then

$$\text{Original case: } P_{\text{loss}} = 10 \cdot (6.99)^2 = 489 \text{ W}$$

$$\text{After compensation: } P_{\text{loss}} = 10 (4.76)^2 = 227 \text{ W}$$

As we see, to do a certain job we are using 1000 W, but causing a power loss of 489 W in the first case, while to do the same job, we will cause a power loss of 227 W after compensation. This is less than half the loss caused originally.